

# VHDL Language

## *Application in the programmable components of type FPGA*

### **Contents :**


- I. Constitution of a VHDL program
- II. Declaration of entity
- III. Declaration of the architecture
- IV. Types of descriptions
- V. Process
- VI. Syntactical tools
- VII. Examples

# VHDL Language

## **I – Constitution of a VHDL program**

- Standardized language IEEE-1076 in December, 1987
- Unique language allowing a behavioral description of a system without taking into account the characteristics of the component in which the system will be implanted. It is thus independent from processes and technologies.
- The choice of the component is made at the last stage of the study of the system


# VHDL Language

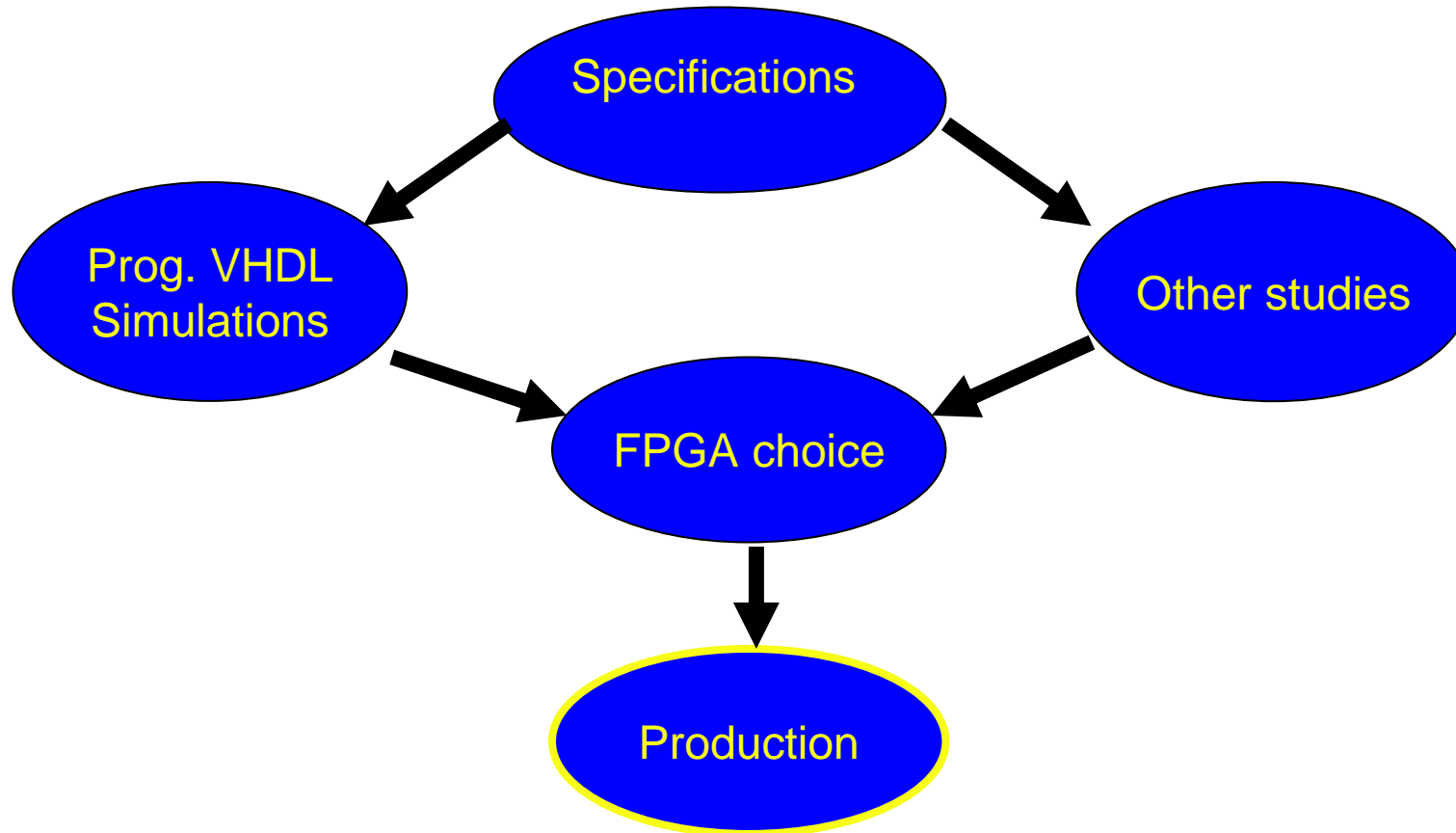

# VHDL Language

## Entity : IN /OUT descriptions

The program is comprised of two parts:

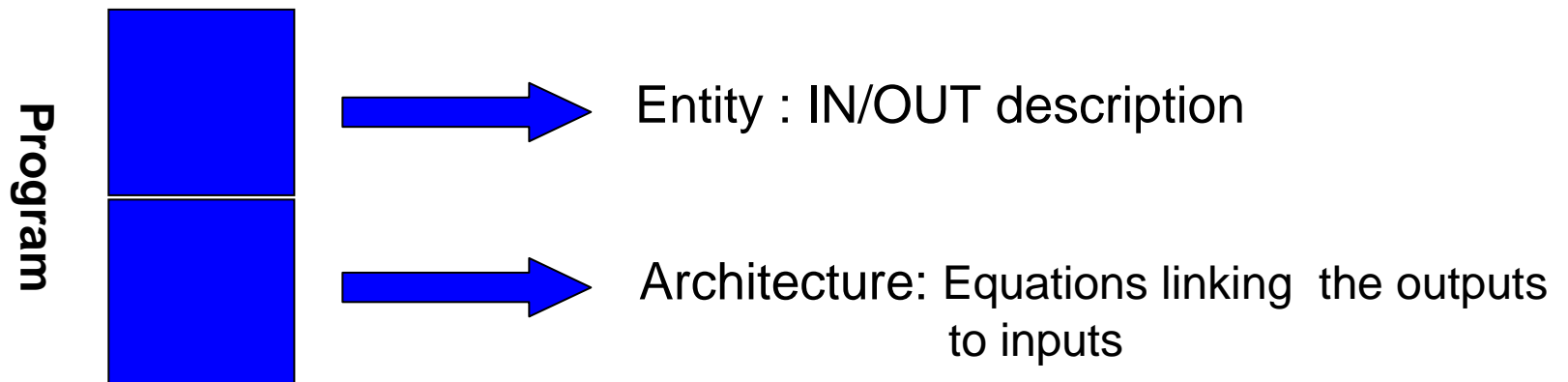

# VHDL Language

## II – Entity declaration

- It contains libraries or packages for the the program syntax

Package examples :

➡ ieee.std\_logic-1164.all → Libraries of the logical functions  
(or, and, xor, .....


➡ ieee.std\_arith.all → Mathematical library (+, -)

- It defines inputs and outputs: the ports of system

# VHDL Language

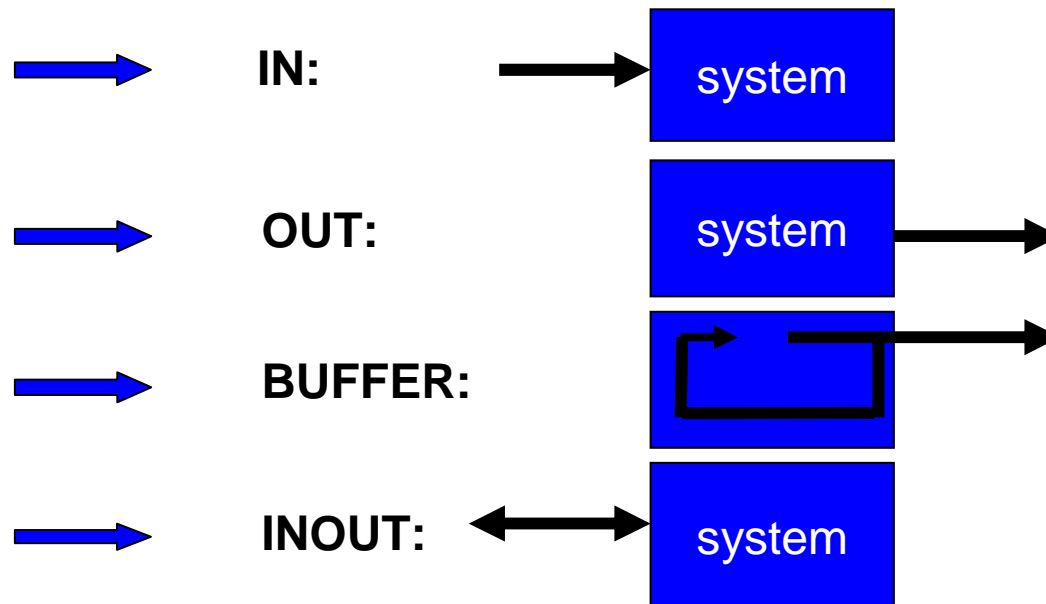
## Definitions of the ports of the system:

Inputs or outputs can have several "directions"



# VHDL Language

 
## Example of description of an entity: comparator



```
library ieee; Use ieee.std_logic_1164.all;  
  
entity comparer is  
    port (A,B: in std_logic;  
          Y: out std_logic);  
end comparer;
```

# VHDL Language

1st possibility:

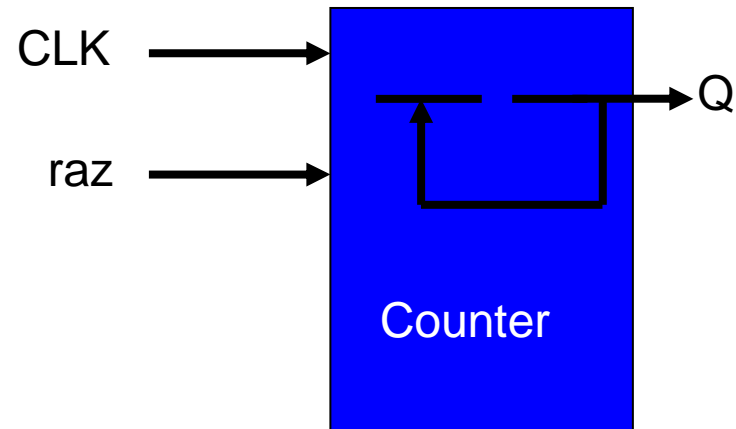

library ieee;

Use ieee.std\_logic\_1164.all;

entity counter is

port ( CLK,raz: in std\_logic;

Q:buffer std\_logic\_vector (2 downto 0));

end counter;

# VHDL Language

## 2<sup>nd</sup> possibility:

```
library ieee;  
Use ieee.std_logic_1164.all;  
  
entity counter is  
    port ( CLK,raz: in std_logic;  
          Q:out std_logic_vector (2 downto 0));  
end counter;
```

*NB: The feedback (present state, future state) will be assured by one internal variable defined as an internal signal (of which we do what we wish) in the architecture (cf continuation)*

# VHDL Language

## III - Declaration of the architecture

- The architecture defines the equation linking the outputs to the inputs of the system

**It describes the functioning of the ENTITY**

- The language VHDL authorizes several levels of description:

- Low level (structural): description by use of primitive (gates AND, OR)
- High level (behavioral): description of the feature in reference to the underlying material

# VHDL Language

## IV – Types of descriptions

- The behavioral descriptions facilitate the mobility (independence of the technology and the component)
- The structural descriptions facilitate the efficiency (optimization of the produced function):
  - = > optimization manual worker of the compilation
  - = > description by blocks thus easier debugging
- At any time (including inside same architecture) it is the designer who decides on the level of description.

# VHDL Language

## Various architectures:

### ■ Behavioral description



```
library ieee;  
Use ieee.std_logic_1164.all;  
  
entity comp is  
    port (A,B: in std_logic;  
          Y: out std_logic);  
end comp;
```

```
Architecture ARCH1 of comp is  
begin  
    Y<= '1' when (A=B) else '0';  
End ARCH1;
```

```
Architecture ARCH2 of comp is  
begin  
    Y<= not (A xor B);  
End ARCH2;
```

# VHDL Language

## ■ Structural description:

```
library ieee;  
Use ieee.std_logic_1164.all;  
entity comp is  
    port (A,B: in std_logic;  
          Y: out std_logic);
```

```
end comp;
```

```
Architecture ARCH3 of comp is
```


```
Signal I:bit;
```

```
begin
```

```
    IC0: xor2 port map (A=>A,B=>B,S=>I);
```

```
    IC1: inv port map (I=>E,S=>Y);
```



```
End ARCH3;
```

 

***NB: Xor and inv are supposed as being already compiled and declared in one package***
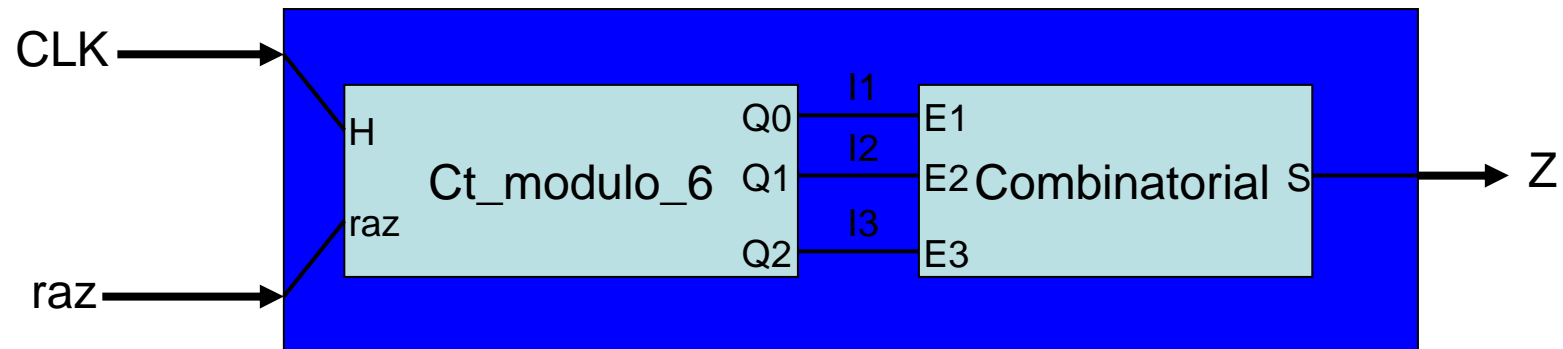 
# VHDL Language

- Other examples of a structural description: synthesis of a signal Z from a clock H



# VHDL Language

```
library ieee;
Use ieee.std_logic_1164.all;
entity signal_Z is
    port (CLK,raz: in std_logic;
          Z: out std_logic);
end signal_Z;
Architecture ARCH of signal_Z is
Signal I1,I2,I3:bit;
begin
    IC0: ct_modulo_6 port map (CLK=>H,raz=>raz,Q0=>I1,Q1=>I2,Q2=>I3);
    IC1: combinatorial port map (I1=>E1,I2=>E2,I3=>E3,S=>Z);
End ARCH;
```

***NB: With XILINX, we associate symbols with every file VHDL representing a function. Then We connect them then in a graphic way in a schematic window.***

# VHDL Language

## V - Process

The process allows the description of synchronous sequential systems


➔ The process is the main construction allowing this description  
***NB: The synchronous character of the description authorizes a parallelism of the operations. It results from in a gain of speed.***

- The process is located in the architecture
- Inside a process, the instructions run in a sequential way
- Outside of a process the operations run simultaneously
- A process runs in every change of state of the input signals to which it is sensitive. We create an inventory of these signals. It is entitled " list of sensibilities "

# VHDL Language
 
## Example of description of a sequential system: counter

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
entity counter is
    port (H: in std_logic;
          Q: buffer std_logic_vector (2 downto 0));
end counter;
Architecture ARCH of counter is
begin
    process ( H )
    begin
        if (H' event and H = '1') then
            Q <= Q+1;
        end if;
    end process;
end ARCH;
```



Counter on

# VHDL Language

## VI - Syntactical tools

- Logical operators:
  - AND { Y <= A and B; }
  - OR { Y <= A or B; }
  - NOT { Y <= NOT (A); Y <= NOT (A AND B); }
  - NAND { Y <= A NAND B; }
  - NOR { Y <= A NOR B; }
  - XOR { Y <= A XOR B; }
- Instructions in mode contributing (Except process)
  - Assignment <=
  - Conditional assignment <= ... WHEN
  - Selective assignment WITH ....SELECT

# VHDL Language

- Instructions in sequential mode (IN A PROCESS)

assignment <=

Conditional assignment <= .... If...THEN...  
end if;

selective assignment case ....when

LOOP(NEXT,EXIT,FOR...LOOP, WHILE...LOOP

- Arithmetical operators::

sum: +

subtract: -

multiplication: \*

division: /

not equal: /=

equal =


.....

# VHDL Language

## VI – Examples of VHDL descriptions
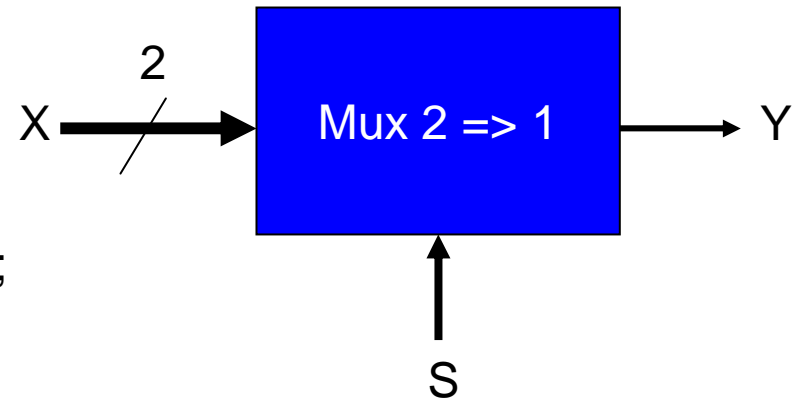
### *Example n°1: Multiplexer 2=>1*


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
entity mux2_1 is
    port (X: in std_logic_vector(1 downto 0);
          S: in std_logic;
          Y: out std_logic);
end mux2_1;
Architecture ARCH of mux2_1 is
begin
    with S select
        Y <= X(0) when '0',
            X(1) when others;
end ARCH;
```



# VHDL Language
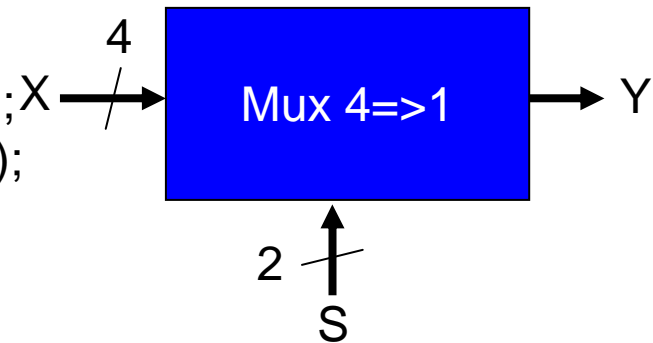
## Exemple n°2: Multiplexer 4=>1

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
entity mux4_1 is  
  port (X: IN std_logic_vector(3 downto 0);  
        S: IN std_logic_vector(1 downto 0);  
        Y: out std_logic);  
end mux4_1;
```



# VHDL Language

architecture ARCH of mux4\_1 is


```
begin
  seq:process(X,S)
  begin
    case S is
      when "00" => Y <= X(0);
      when "01" => Y <= X(1);
      when "10" => Y <= X(2);
      when others => Y <= X(3);
    end case;
  end process seq;
end ARCH;
```

# VHDL Language
 
## Exemple: counter modulo 4

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
entity cpt_4 is  
    port (H,raz: in std_logic;  
          Q: out std_logic_vector(1 downto 0));  
end cpt_4;
```

```
Architecture ARCH of cpt_4 is  
    signal etat: std_logic_vector(1 downto 0);  
    begin  
        Q<=etat;  
        process (H,raz)  
            begin  
                if (H' event and H = '1') then  
                    if raz = '1' then etat <= "00";  
                    else etat <= etat+1;  
                    end if;  
                end if;  
            end process;  
        end ARCH;
```



Definition of a signal: variable interns allowing to define releases from sequential releases(cf example synthesis of the signal Z taken out: Z out sequential: Q of the counter)

# VHDL Language

## Additive: instruction ELSIF

Used in the architecture when several conditions take place

NB: placed after an if, this instruction is not finished by an end if

Architecture ARCH of system is

```
begin
  process (H)
    begin
      if (H' event and H = '1') then
        if ..... then..... ;
        elsif.....then..... ;
      end if;
    end if;
  end process;
End ARCH;
```